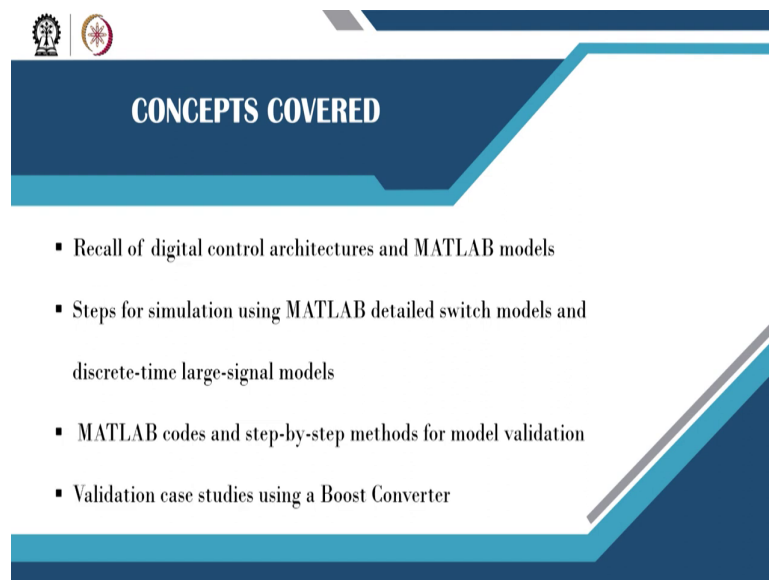


Digital Control in Switched Mode Power Converters and FPGA-based Prototyping
Prof. Santanu Kapat
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Module - 04
Modeling Techniques and Mode Validation using MATLAB
Lecture - 36
Validation of Discrete-Time Large-Signal Models using MATLAB-II

Welcome back. So, this is the second part of you know a lecture, you know we are continuing from the previous lecture, where we are going to validate Discrete Time Large Signal Model and here we are considering a boost converter case study.

(Refer Slide Time: 00:36)




The slide features a dark blue header with the text 'CONCEPTS COVERED' in white. Below the header is a list of four bullet points. The slide is decorated with geometric shapes in shades of blue and grey, and includes two small circular logos in the top left corner.

- Recall of digital control architectures and MATLAB models
- Steps for simulation using MATLAB detailed switch models and discrete-time large-signal models
- MATLAB codes and step-by-step methods for model validation
- Validation case studies using a Boost Converter

So, here we are again talking about digital control architecture, particularly the voltage mode control and its MATLAB model, we will show steps for simulation using MATLAB detailed switch model and discrete time large signal model.


Then we will talk about the MATLAB course and step-by-step method for model validation, and we will take a few case studies of a boost converter digital voltage mode control.

(Refer Slide Time: 00:58)

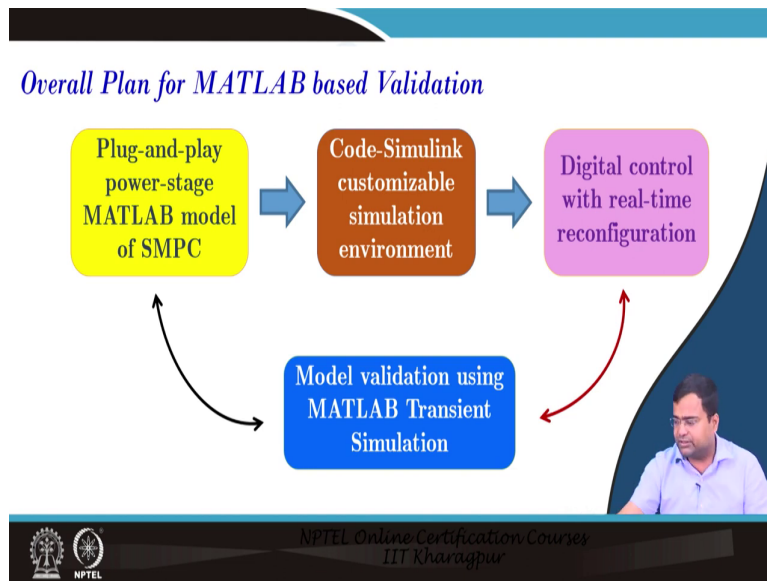

So, here is the overall plan again the plug-and-play power stage model MATLAB model of the boost converter, then we will have a code Simulink customizable model and then we can also have a Simulink model for the digital controller, and finally, we want to validate our discrete-time large signal model with the actual switch simulation.


(Refer Slide Time: 01:16)

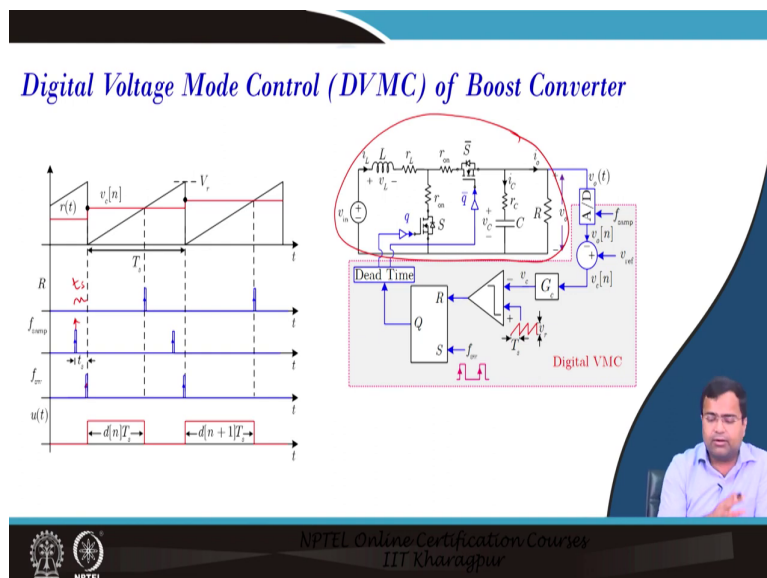

So, here we are talking about it is the same as the previous lecture, here we had only we have changed the boost converter power stage ok. And everything else is the same as the previous one. So, here we are first taking the sample, and in this sample, we are providing some delay

here t_s , after which we are turning on the PWM switch because it is running under trailing edge modulation. So, this delay is to account for the ADC conversion and the computational time; and that we have discussed.

(Refer Slide Time: 01:45)

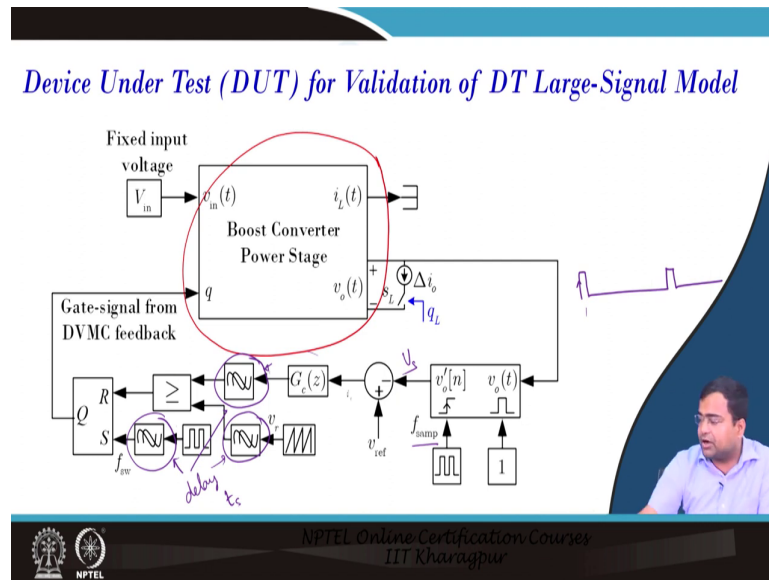

And we have also discussed, the power stage. So, this is the boost converter power stage, we have captured it as if like we are going to implement it in Simulink, and then here we have considered the delay. So, these are the ok let us use a different color. So, we are talking about a delay. So, this is one block, this is another block and this is another block. So, these are our delays.

So, the delay is t_s . So, this block and this block are the delays. And here we are using a sampling clock, which is a fixed frequency clock like this, and every rising edge of this clock with sample and the output voltage sample.


Then it is computed through this you know the PID controller, then it is delayed by this signal. So, all clocks are delayed. So, that they are synchronized. So, there the PWM action starts.

(Refer Slide Time: 02:38)

Validation of DT Large-Signal Model under Closed Loop

a) Using actual switch simulation

1. Provide initial conditions for $v_C(t)$ and $i_L(t)$
2. Do not turn on S_L for 1 ms and let the converter reach steady-state
3. Apply a load step
4. Capture time domain data and store as v_o and i_L



NPTEL Online Certification Courses
IIT Kharagpur

Now we have discussed the validation state. So, we have to first run the actual switch simulation, where we have to set the initial condition of the capacitor voltage and the inductor current. Then we will run for one load resistance for some instant of time, here we are talking about 1 millisecond, but again it is flexible, then the converter will reach a steady state, then we will apply a load step; that means, we are changing the load resistance from r_1 to r_2 .


And then, it will create a virtual load step and we will capture the all-time domain data output voltage inductor current and other data in the workspace.

(Refer Slide Time: 03:12)

Validation of DT Large-Signal Model under Closed Loop (contd...)

b) Using DT large-signal model

1. Provide initial conditions for $v_C(t)$ and $i_L(t)$ same as the switch simulation
2. Let the DT large-signal model run for 1 ms
3. Capture $v_o(t)$ and $i_L(t)$ for every sampling cycle until 1 ms



NPTEL Online Certification Courses
IIT Kharagpur

Then we will run a discrete time large signal model, and I will go to the MATLAB case study, we will keep the same initial condition of the capacitor voltage and the inductor current, the same as the switch simulation. Then we will run the discrete-time large signal model and we will run for 1 millisecond, then we will capture all the v_0 inductor current for every sampling cycle until 1 millisecond.

(Refer Slide Time: 03:34)

Validation of DT Large-Signal Model under Closed Loop (contd...)

b) Using DT large-signal model

4. Change the load resistance at 1 ms to emulate a load step
5. Capture $v_o(t)$ and $i_L(t)$ for every sampling cycle until the end time same as simulation run time
6. Compare the captured data of v_o & i_L for DT large-signal validation

NPTEL Online Certification Courses
IIT Kharagpur

Then again we will change the load resistance from r_1 to r_2 , I will come to that. Then again we will run our discrete-time larger signal model, and capture the v_0 and i_L data for every cycle.

Because we are talking about the discrete-time large signal model; that means if you let us say we are talking about output voltage waveform like this if you are talking like this if this is your you know. So, this is your sampling instant; that means, your sampling clock, and this is your switching clock right? So, we are talking about the model, which means, there will be another. So, this will be the $f_{switching}$ $f_{sampling}$.

So; that means, these two are the point, we are talking about the discrete-time models. So that means, we are capturing the sample at every data we are capturing the value of the like a voltage and current waveform, at the sampling instant. Then we will compare the captured data of the output voltage and inductor current of the discrete-time model, which will be compared with the actual switch simulation.


(Refer Slide Time: 04:35)

Steps to Verify Large-Signal DT Model using MATLAB

```
boost_conv_DVMC_simulation.m
clear; close all; clc;
%% Setting parameters
boost_parameter;
DCM_En=0;
N_tran=500; T_tran=2*N_tran*T;
t_start=0; t_sim=T_tran;
%% Controller parameters
Kp=8; Ki=0.7; Kd=(1*C)/T;
t_s=0.1*T;
V_m=10; R1=10; R2=2; R=R1;
I_L_int=0; V_c_int=4.99;
V_s_int=V_c_int; V_integral=0;
.....

boost_parameter.m
L=2e-6; % inductance
C=100e-6; % output capacitance
T=2e-6; % switching time period
r_L=10e-3; % inductor DCR
v_d=0*0.7; % diode voltage drop
r_1=5e-3; % LS MOS on resistance
r_d=5e-3; % HS MOS on resistance
r_C=5e-3; % capacitor ESR
Vin=3.3; % input voltage
Vref=5; % ref. output voltage
```

$V_{ref} = 5V$
 $V_{in} = 3.3V$



NPTEL Online Certification Course
IIT Kharagpur


And again the seminar code, where we have discussed for the buck, only here it is a boost converter, for boost converter we have taken L equal to 2 micro henry, capacitor to be a 100 micro farad, 2 microsecond time period then all the parasitic.

Then again we are running for the first 500 cycles for 1 load resistance r 1, then another 500 cycles for another load resistance r 2, that is why I have taken the total transient time total is two times the 500 cycle; that means, N tran into t that is the time period.

And total simulation time is a T tran and we are setting some arbitrary Kp Ki Kd value in the discrete domain, and we are setting a delay of T by 10 ok. And the ramp voltage of 10 volt initial load resistance of 10 ohm, the final load resistance of 2 ohm, and the output voltage whereas, were desired output voltage V ref we have taken to be 5 volt, is written and the input voltage we have taken V in to be 3.3 volt, but again, it is flexible we can change it.

(Refer Slide Time: 05:38)

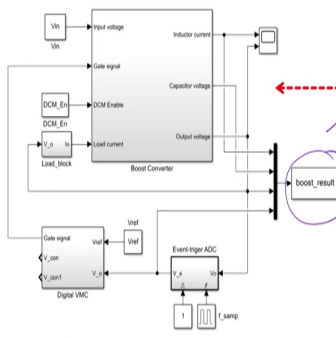Steps to Verify Large-Signal DT Model using MATLAB (contd...)




```
boost_conv_DVMC_simulation.m
.....
sim('boost_converter_DVMC.slx');
t=boost_result.time; t_scale=t*1e3;
x=boost_result.data; i_L=x(:,1);
V_cap=x(:,2);
V_o=x(:,3); V_s=x(:,4);
%% Plot subroutine
plot_boost_simulation;
```

NPTEL Online Certification Courses
IIT Kharagpur

Next, this is the overall model, and I will go to the model very soon, we are running the Simulink model from the dot m file, using this command, then this is storing all the data in the workspace; then we are calling time vector and the data vector, data it is a structure, then we will take individual vector like a current, capacitor voltage, output voltage, sample voltage and so on. And then we will use the plot command.

(Refer Slide Time: 06:02)

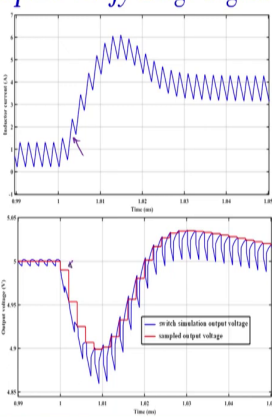Steps to Verify Large-Signal DT Model using MATLAB (contd...)



```
boost_conv_DVMC_simulation.m
.....
sim('boost_converter_DVMC.slx');
t=boost_result.time; t_scale=t*1e3;
x=boost_result.data; i_L=x(:,1);
V_cap=x(:,2);
V_o=x(:,3); V_s=x(:,4);
%% Plot subroutine
plot_boost_simulation;
```

NPTEL Online Certification Courses
IIT Kharagpur

Then if we plot it, it will look like this. So, this is the actual switch simulation and here the red one is tracking the sample voltage.

But your actual switching instant is different and we will go to the case study soon.

(Refer Slide Time: 06:15)

Steps to Verify Large-Signal DT Model using MATLAB (contd...)

boost_DT_LSM_TE.m

```

clear
boost_parameter;
Kp=8; Ki=0.7; Kd=(1*C)/T;
t_s=0.1*T; N_m=10; Rl=10;
R2=2; R=Rl; N_tran=500;
boost_DT_model_matrices;
.....

```

Command

$R_2 = R_l$

boost_DT_model_matrices.m

```


alpha=R/(R+r_C); r_e=(r_l+r_L);
T_s=t_s; I_den=[1 0; 0 1];

%% Define system, input and output matrices
A_on=[-r_e/L 0; 0 -alpha/(R*C)];
A_off=[-(r_e+(alpha*r_C))/L -alpha/L;
        alpha/C -alpha/(R*C)];
B=[1/L; 0];
C_on=[0 alpha];
C_off=[r_C*alpha alpha];

```

A_{on}
A_{off}
B
C_{on}
C_{off}

$C_{off} = \begin{bmatrix} \alpha r_c & \alpha \\ 0 & \alpha \end{bmatrix}$
 $C_{on} = \begin{bmatrix} 0 & \alpha \end{bmatrix}$



NPTEL Online Certification Courses
IIT Kharagpur

Then we have to run, for the discrete-time large signal model. So, the discrete-time large signal model is the file name. So, we will first clear, then we will have the boost parameter. Again this parameter we can comment, we can comment; because the only thing we have to define is the N tran because that is not there in your switch simulation. I think it is there; in the switch simulation. So, N tran is already defined. So, these are all you can comment on, you can comment on this signal.

Then, once initially it is running r l, r l load resistance. So, r l is what? 10 milli ohm. So, the boost parameter has to model matrix has to be set accordingly. So, here initially it will take r equal to r l, the first 500 cycles, then it will enter into this matrix, where the matrix will be set alpha this thing and we know for a boost converter, what are the on-state matrix, what are the off state A matrix; they are different.

And we know the B matrix is the same for the boost converter, because the input voltage is connected all the time, and then it has an output matrix that is different for on-state and off-state. So, the on-state output and off-state output matrix are shown here.

And because they are different, you can see this is the additional term, which will be extra in the off state; that means, our off state matrix is alpha you know r c, alpha r c ok. So, it is the alpha r c and it is alpha and on stage, the matrix is simply 0 alpha. So, this term is extra every

switching transition will change and that will make the boost converter has a discontinuous output voltage ripple, at every switching transition because of this discontinuity.

(Refer Slide Time: 08:08)

Steps to Verify Large-Signal DT Model using MATLAB (contd...)

boost_DT_LSM_TE.m


```

.....
i_L_n=L_L_int; v_cap_n=V_c_int;
x_n=[i_L_n; v_cap_n];
V_o_s=C_off*x_n; Vsam=v_cap_n;
V_intg_int=0; Ve_int=0;
t1=0; t1_scale=t1*1e3;

figure(1)
plot(t1_scale,x_n(1),'o','Linewidth', 2); hold on; grid on;

figure(2)
plot(t1_scale,Vsam,'o','Linewidth', 2); hold on; grid on;
.....

```



NPTEL Online Certification Courses
IIT Kharagpur

So, now we have the initialization value it will take from the Simulink, the switch simulation, and it will run for you know whatever times were are set already in the switch simulation. Then it will plot the discrete time value, and then we are going to match.

(Refer Slide Time: 08:31)

Steps to Verify Large-Signal DT Model using MATLAB (contd...)

boost_DT_dynamics.m

```

for n=0:N_tran-1
figure(2)
plot(t1_scale,Vsam,'o','Linewidth', 2); hold on; grid on;
Ve=(Vref-Vsam);
V_intg=V_intg_int+(Ki*Ve); V_intg_int=V_intg;
V_der=Kd*(Ve-Ve_int); Ve_int=Ve;
Vcon=(Kp*Ve)+V_intg+V_der; D_temp=Vcon/V_m;

if D_temp<0
D=0;
elseif D_temp>1
D=1;
.....

```

boost_DT_LSM_TE.m


```

.....
%% DT Large-Signal Model
boost_DT_dynamics;
R=R2; N_tran=500;
boost_DT_model_matrices;
V_o_s=C_off*x_n; Vsam=
V_o_s;
boost_DT_dynamics;

```

Handwritten notes:

- N_{tran} 0 to $N_{tran}-1$
- $U_2(n) = U_2(n-1) + K_i V_e(n)$
- $U_3(n) = K_d (V_e(n) - V_e(n-1))$
- $U_4(n) = K_p V_e(n)$
- $U(n) = U_2 + U_3 + U_4$



NPTEL Online Certification Courses
IIT Kharagpur

Now once we call; that means, it is continuing the large signal model, then next what is inside the boost dynamics? So it is running from totally for N tran time; that means, it will call from 0 to N tran minus 1 and that is exactly what is here. So, what it will do will first compute the PID controller. This is the proportional control, this is integral and this is the derivative.

And the integral control is nothing but the previous; that means, we know that u I of n is integral, will be u I of n minus 1 plus K i into V e of n ok and this is the previous value. Similarly, the u I D derivative part of n will be equal to K d into V e n minus V e n minus 1 ok.

And the proportional part is very common, it is simply K p into V e n and the total sum will be added u P plus u I plus u D all are n ok.

(Refer Slide Time: 09:50)

Steps to Verify Large-Signal DT Model using MATLAB (contd...)

boost_DT_dynamics.m *N_{tran}*
0 to N_{tran}-1

```

for n=0:N_tran-1
figure(2)
plot(tl_scale,Vsam,'o','Linewidth',2); hold on; grid on;
Ve=(Vref-Vsam);
V_intg=V_intg_int+(Ki*Ve); V_intg_int=V_intg;
V_der=Kd*(Ve-Ve_int); Ve_int=Ve;
Vcon=(Kp*Ve)+V_intg+V_der; D_temp=Vcon/V_m;

if D_temp<0
D=0;
elseif D_temp>1
D=1;
.....

```

boost_DT_LSM_TE.m

```

.....
%% DT Large-Signal Model
boost_DT_dynamics;
R=R2; N_tran=500;
boost_DT_model_matrices;
V_o_s=C_off*x_n; Vsam=
V_o_s;
boost_DT_dynamics;

```


Handwritten equations:

$$u_d(n) = u_d(n-1) + K_i V_e(n)$$

$$u_d(n) = K_d (V_e(n) - V_e(n-1))$$

$$u_p(n) = K_p V_e(n)$$

$$u(n) = u_p(n) + u_d(n)$$



So, let me write like this. So, you are saying u P n plus u I n plus u D n will be there.


(Refer Slide Time: 10:03)

Steps to Verify Large-Signal DT Model using MATLAB (cont...)

boost_DT_dynamics.m

```
.....
else
  D=D_temp;
end
A_LS=(expm(A_off*(T-(D*T)-T_s)))*(expm(A_on*D*T))*(expm(A_off*T_s));
B1=(expm(A_off*(T-(D*T)-T_s)))*(expm(A_on*D*T))*((expm(A_off*T_s)-I_den)*(inv(A_off))^B;
B2=(expm(A_off*(T-(D*T)-T_s))*((expm(A_on*D*T)-I_den)*(inv(A_on))^B;
B3=((expm(A_off*(T-(D*T)-T_s))-I_den)*(inv(A_off))^B; B_LS=B1+B2+B3;
x_n1=A_LS*x_n+B_LS*Vin;
t1=t1+T; t1_scale=t1*1e3; x_n=x_n1; V_o_s=C_m*x_n; Vsam= V_o_s;
figure(1)
plot(t1_scale,x_n(1),o,'Linewidth',2); hold on; grid on;
end
```


$x_{n+1} = A_{eq} x_n + B_{eq} V_{in}$



Next, this is continuing, now the large signal model will come and we know that X_{n+1} is equivalent to X_n . So, this large signal model is discussed I think in lecture number 34. So, you can check it we are not going to repeat it, and then the B equivalent into V_{in} . So, you have to and the expression of A equivalent is here. So, this is the whole expression, an expression of B equivalent is here which consists of B_1 plus B_2 plus B_3 , where B_1 is written here, B_2 is here, and B_3 is here. So, it is somewhat you know large expression.

Then you will plug in this discrete-time model, and then once you obtain you run the simulation.

(Refer Slide Time: 10:43)

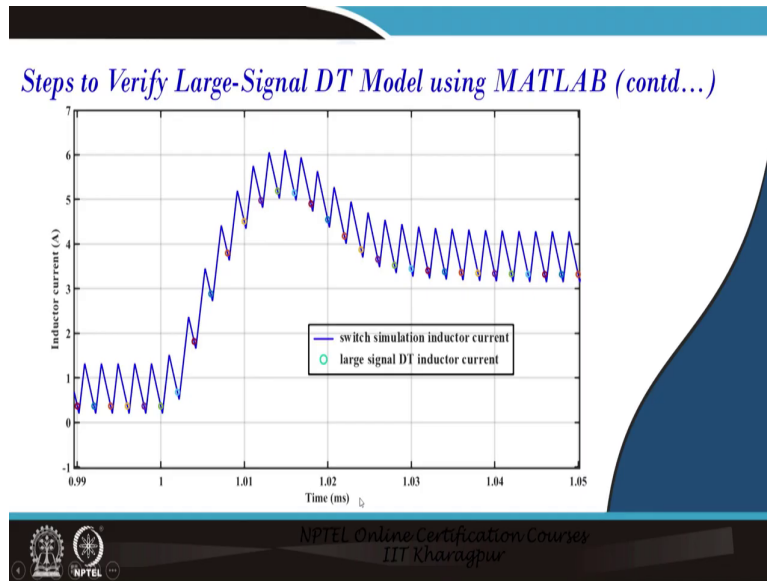

(Refer Slide Time: 10:46)


```
1 %close all; clear;  
2 etc  
3 boost_parameter;  
4  
5 % Kp=S, Ki=0.7, Kd=(1*C)/T, t_s=0.1*T;  
6 % V_m=10, R1=10, R2=2, R=R1, N_tran=500;  
7  
8 boost_DT_model_matrices;  
9  
10 i_L_n=i_L_int; v_cap_n=v_c_int;  
11 x_n=[i_L_n; v_cap_n];  
12 V_o_s=C_off*x_n; Vsam=v_cap_n;  
13 V_intg_int=0; Vc_int=0;  
14  
15 t1=0; t1_scale=t1*1e3;  
16  
17 figure(1)  
18 plot(t1_scale,x_n(1),v,'LineWidth', 2); hold on; grid on;  
19  
20 figure(2)  
21 plot(t1_scale,Vsam,v,'LineWidth', 2); hold on; grid on;  
22  
23 % DT Large-Signal Model
```

And this is the validation. So, let us go to the case study in MATLAB. So, you want to take the MATLAB case study. So, this is the boost converter large signal model, that we have discussed.

(Refer Slide Time: 10:53)


So, this is the switch simulation; we are initializing this.

(Refer Slide Time: 10:57)

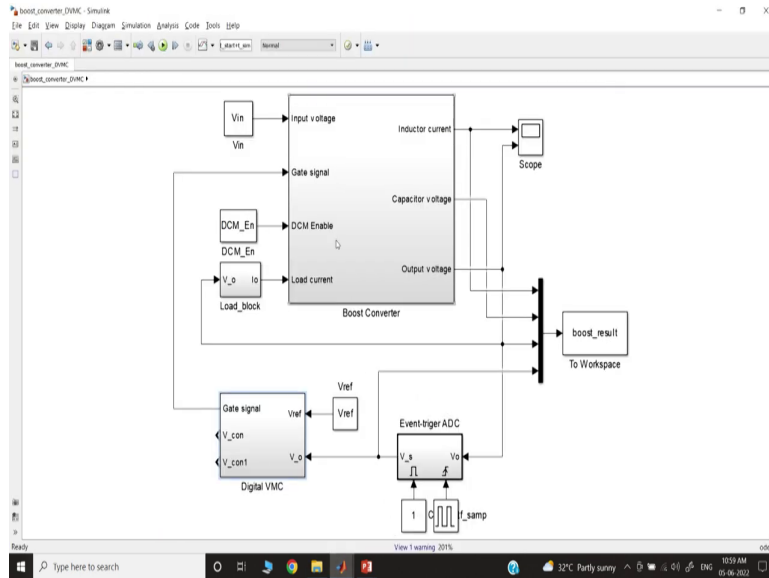

And if you go to the Simulink block of the boost converter. So, this is the boost converter.


(Refer Slide Time: 11:01)

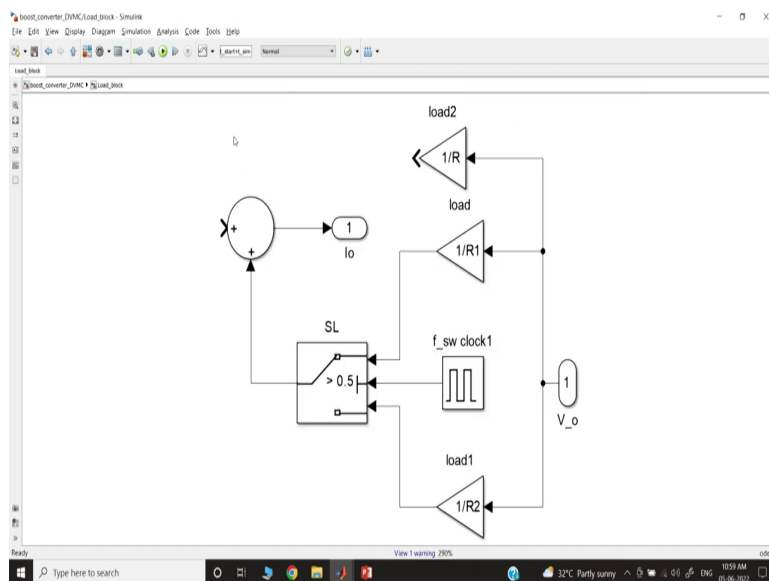

Again this is the load initially it is taking r_1 resistance and then it is taking r_2 resistance. So, r_1, r_2 .


Then it is changing, then what it is taking, if you go up this is the controller.

(Refer Slide Time: 11:17)

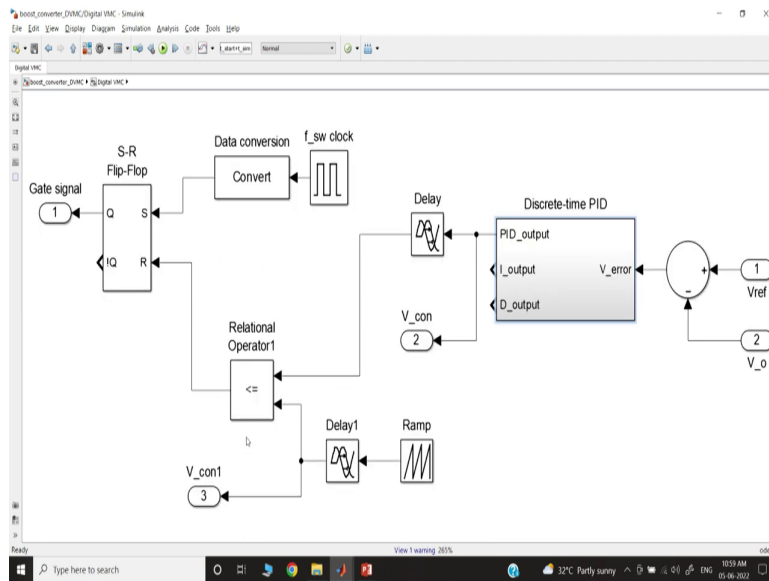


So, if you go inside the controller.

(Refer Slide Time: 11:19)

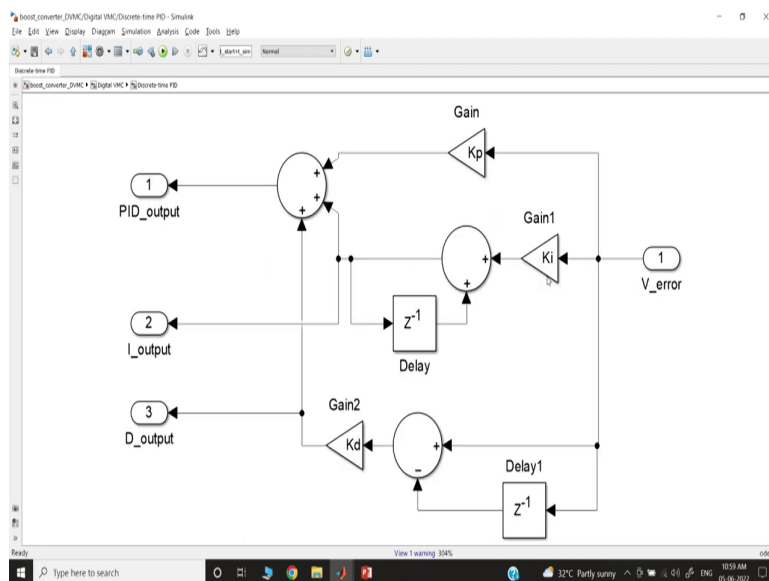


This is the digital PID controller. So, this is the integral discrete time integral control, the discrete-time derivative control, and the proportional control. Next, all controller is added to get the PID control.

(Refer Slide Time: 11:33)

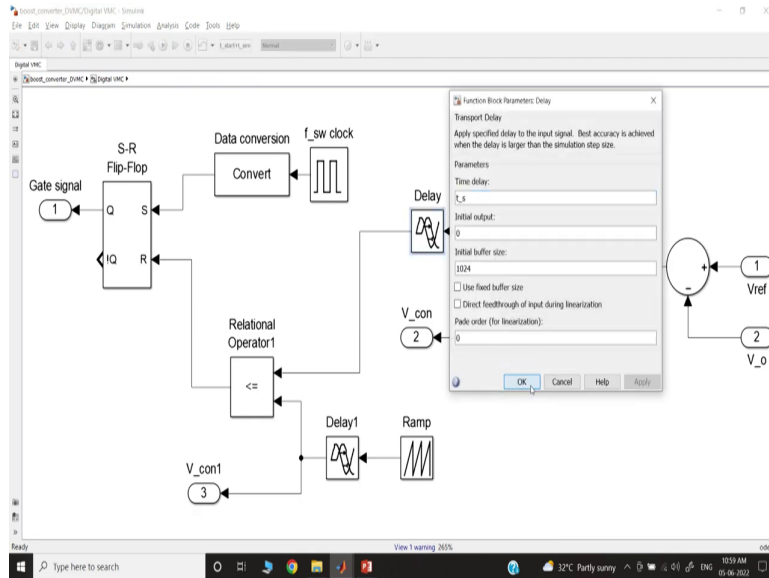


And finally, we will put a delay here t_s and that is the same as the buck converter that we discussed the ramp is also delayed.

(Refer Slide Time: 11:38)

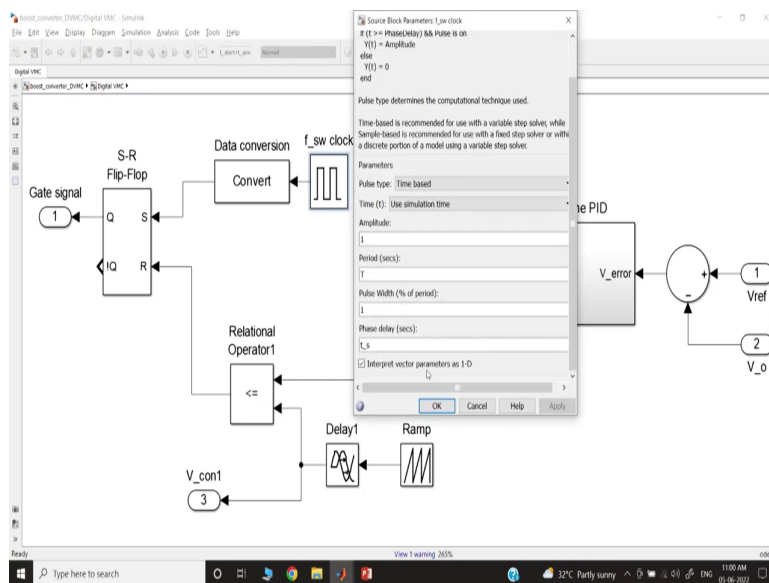


And the clock is delayed here ok.

(Refer Slide Time: 11:44)

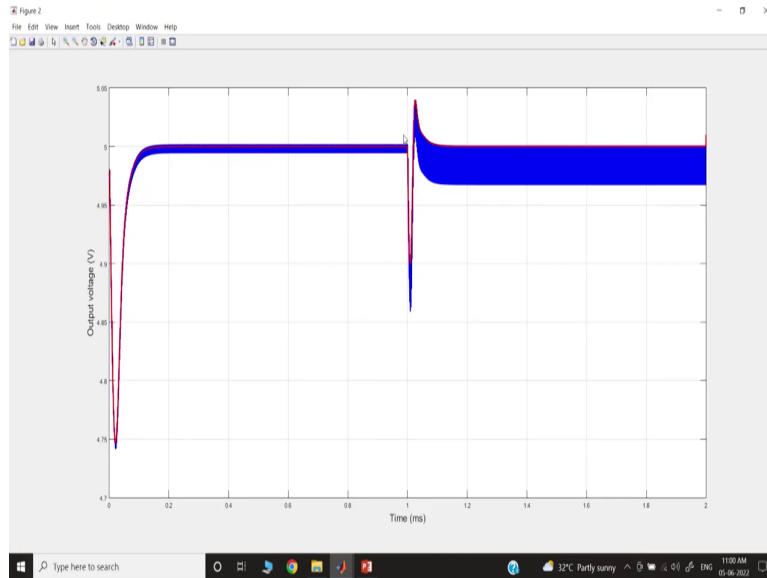


So, now let us go to a case study first. So, we are talking about the load transient case study of a boost converter, and you can see the boost converter you know.

(Refer Slide Time: 11:51)

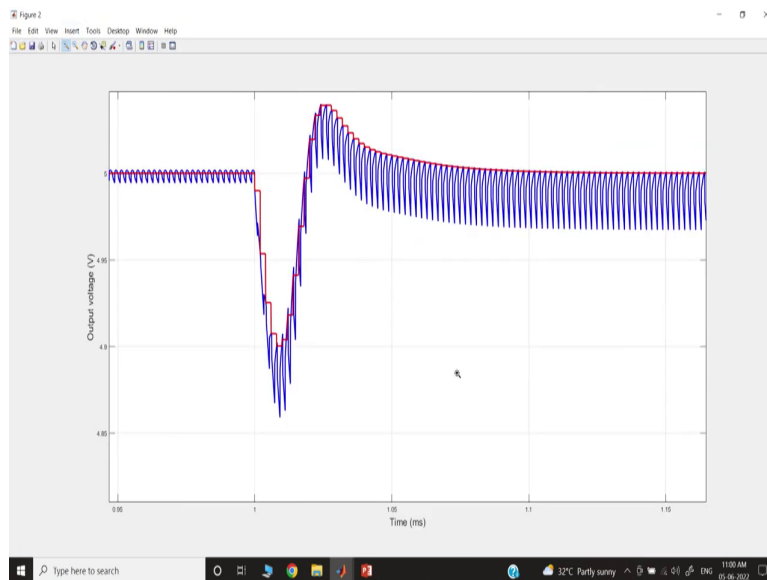


This is the boost converter case study, and this is showing that, if you go to the boost converter, here it is showing from the very initial part.


(Refer Slide Time: 11:58)

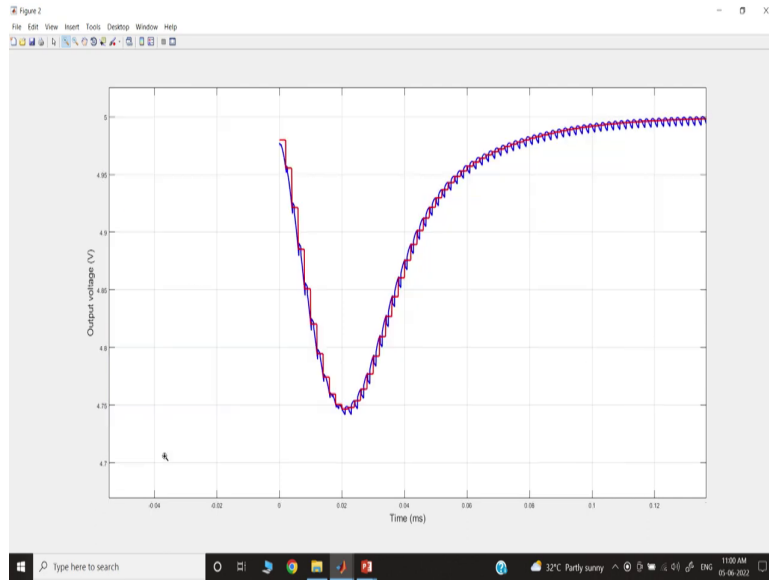

(Refer Slide Time: 12:01)

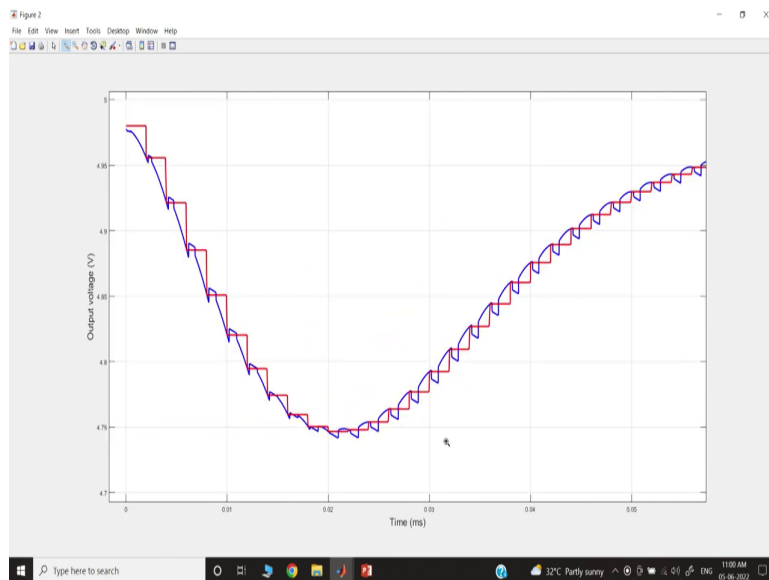


(Refer Slide Time: 12:03)

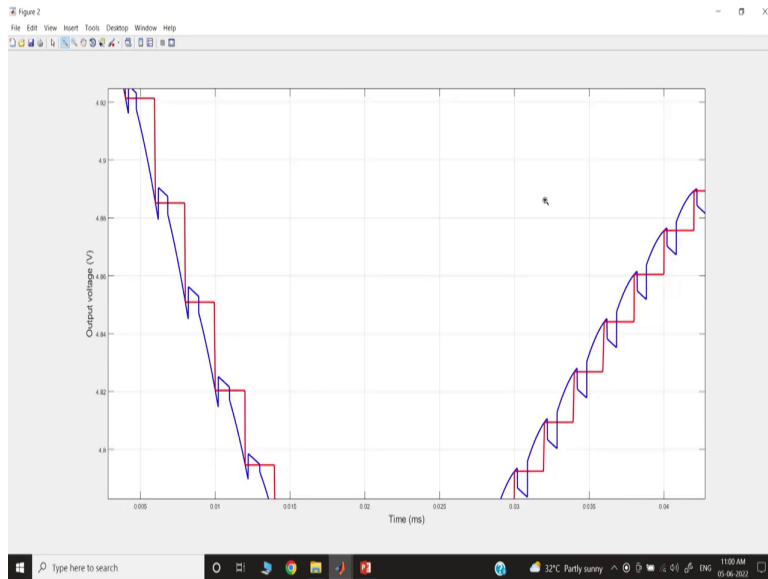


You can show that they are matching quite accurately.

(Refer Slide Time: 12:08)

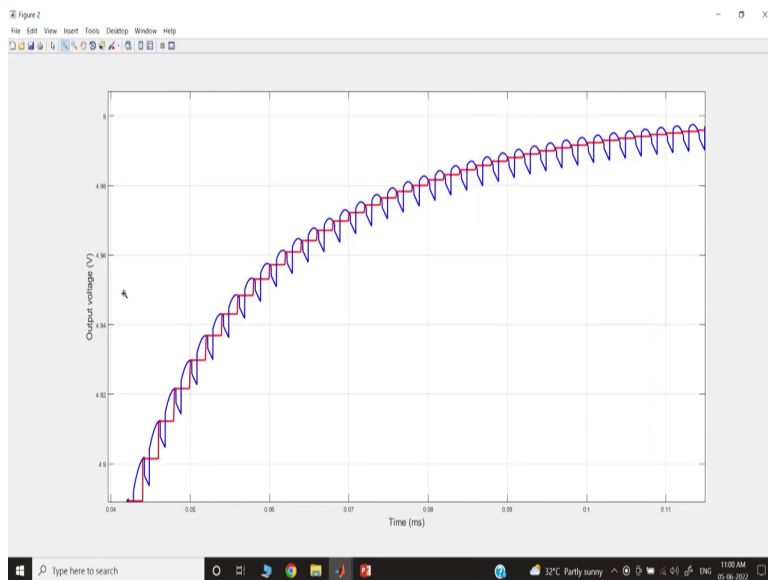

You know if you go like this.


(Refer Slide Time: 12:10)

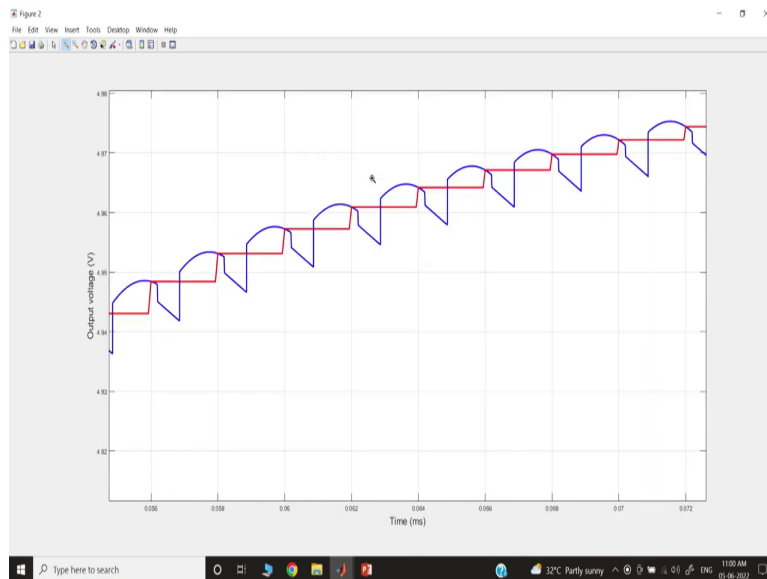

That means, first it is sampling and then it is switching ok.


Now, we want to run for the large signal model. So, let us go to discrete-time large say we are commenting on this gain, but it will take the same controller gain and there is a delay of T_s by 10, now you are running the matching condition.

(Refer Slide Time: 12:27)

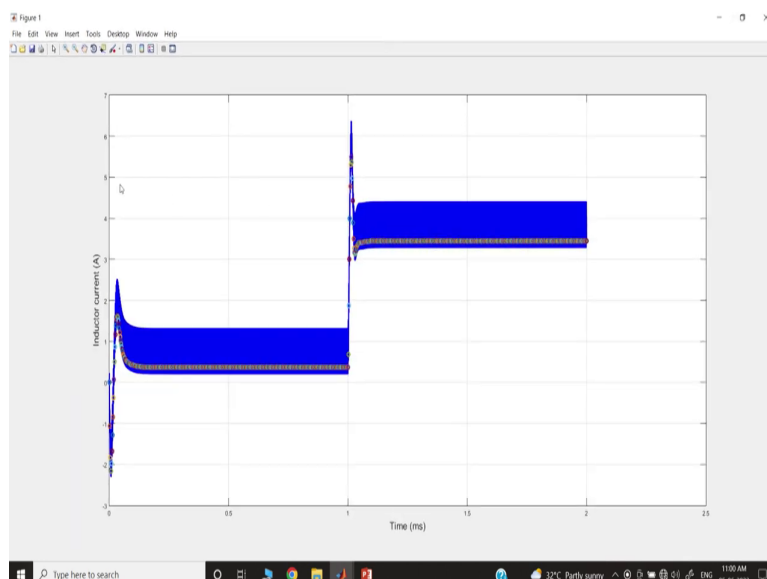


So, first, we will see, that if you take the inductor current waveform ok.

(Refer Slide Time: 12:34)

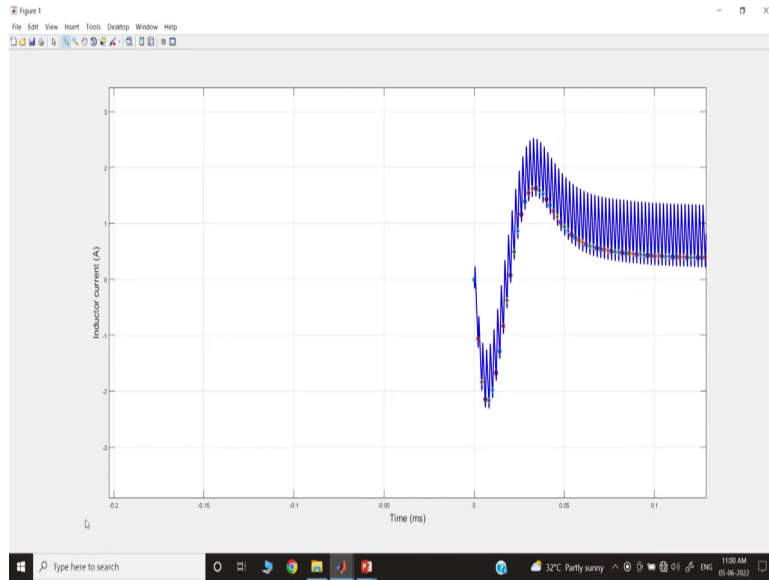


(Refer Slide Time: 12:36)

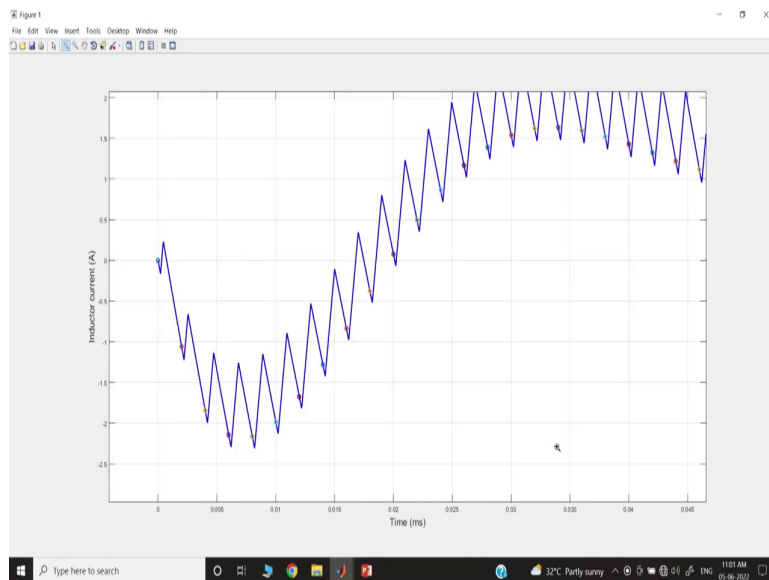


So, inductor current waveform you see they are exactly matching.

(Refer Slide Time: 12:38)

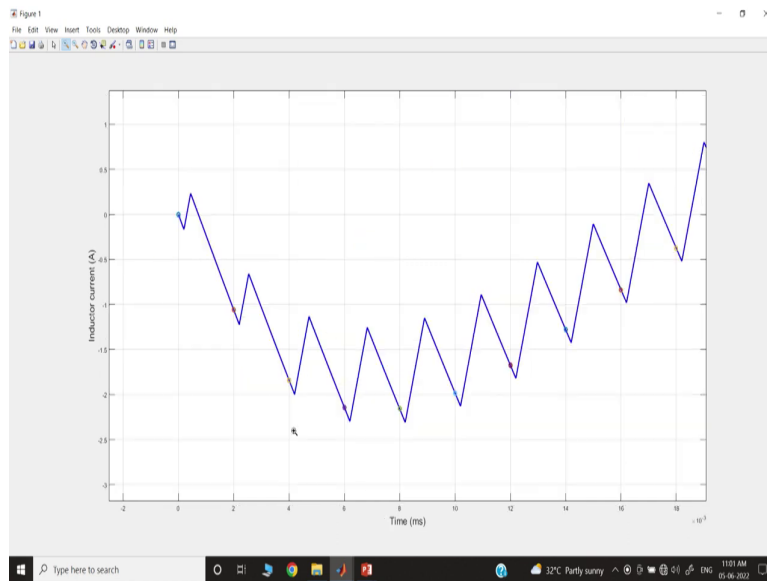

So, first, we are sampling, then after sampling, this switch is turned on.


(Refer Slide Time: 12:42)

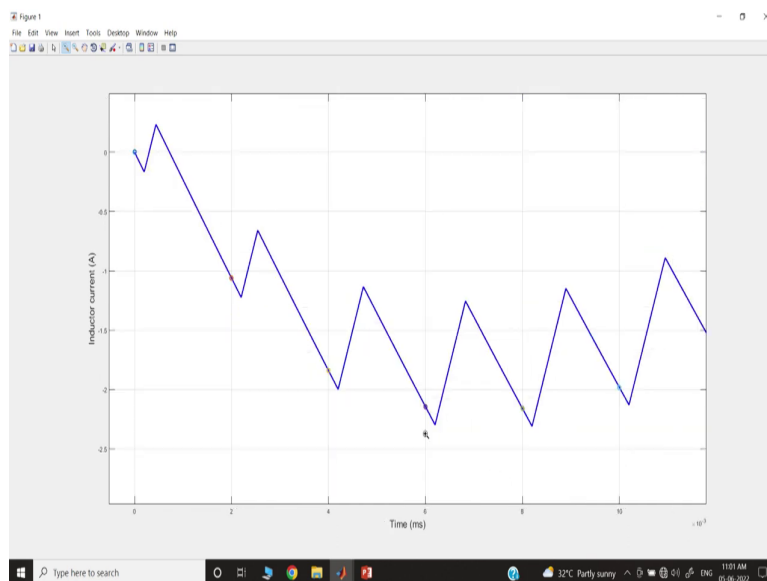


So, they are matching. So, these circles indicate it is coming from a discrete-time model.

And we are sampling at 0, 2 microseconds, and 4 micro. So, every cycle we are sampling, and after its delay, it is switching ok. And then we can also show the output voltage sample.

(Refer Slide Time: 12:56)

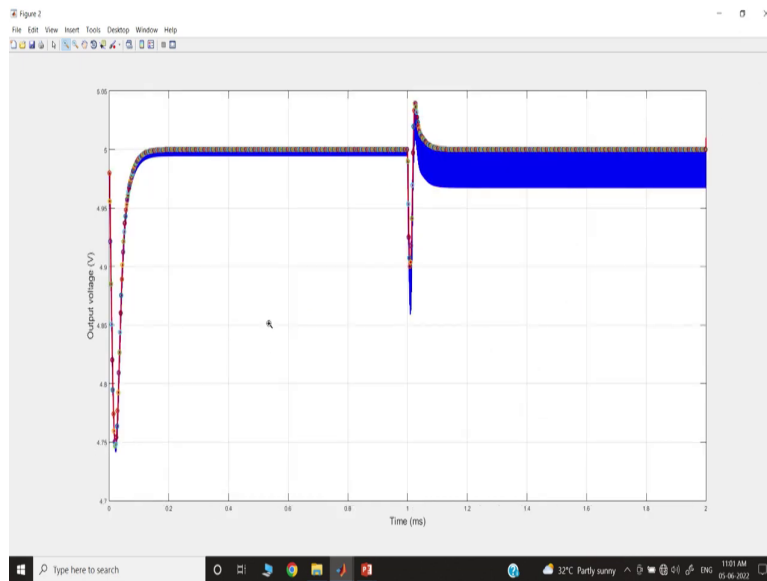

(Refer Slide Time: 12:58)

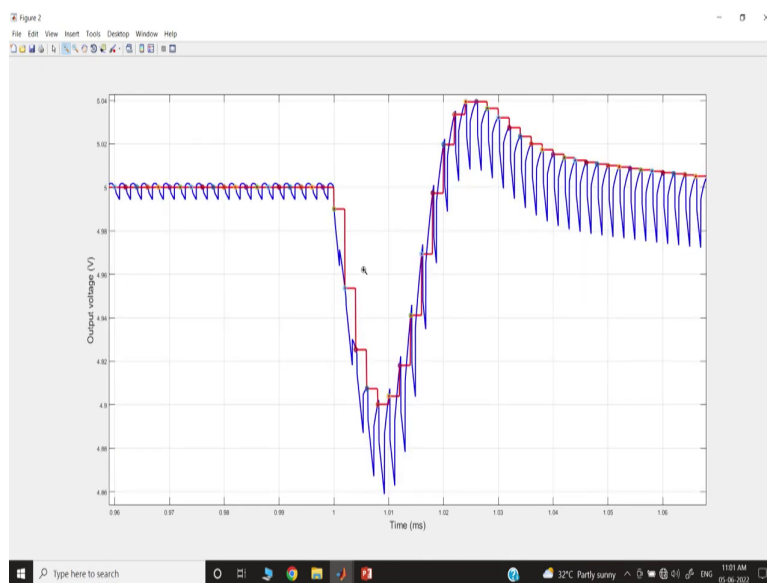

So, if you take the transient portion.

(Refer Slide Time: 13:01)



You can see after the transient.

(Refer Slide Time: 13:03)



The model indicates in this particular circle, it is matching with the actual sample obtained from the switch simulation.

(Refer Slide Time: 13:10)




(Refer Slide Time: 13:12)



So, it is coming from the switch simulation data sample; that means, we can show the case study of the validation case study.

(Refer Slide Time: 13:22)

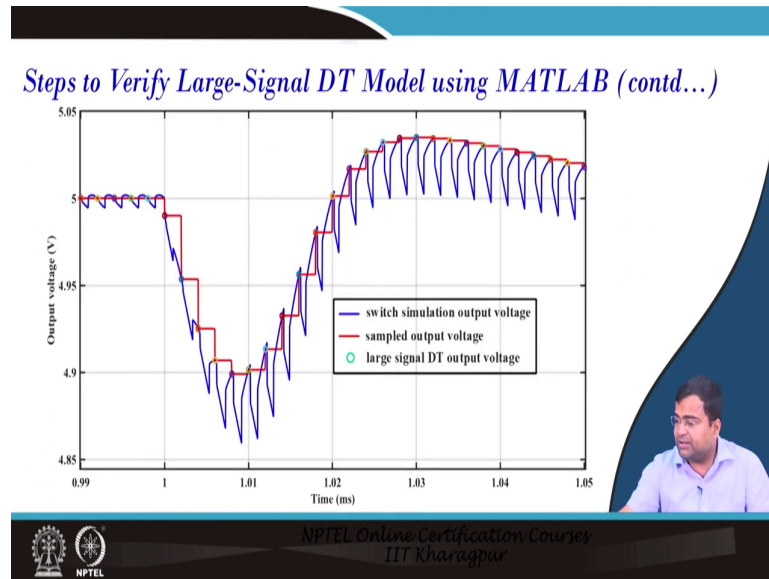

So, we have discussed this validation; that means, these circles are like a large signal model coming between the two subsequent sample points, then the red one is the actual sample coming from the switch simulation and the blue one is the switch simulation the time domain waveform.

(Refer Slide Time: 13:36)

CONCLUSION

- Recall of digital control architectures and MATLAB models
- Steps for simulation using MATLAB detailed switch models and discrete-time large-signal models
- MATLAB codes and step-by-step methods for model validation
- Validation case studies using a Boost Converter

So, in summary, we have discussed digital control architecture and MATLAB model, we have shown the step for simulation using MATLAB detailed switch models and discrete time large signal model, then we have also discussed discrete time MATLAB course and step by step

method for model validation and finally, we have considered from a validation case study using a boost converter.

So, I think these two lectures should be sufficient to understand how to do a validation case study, one can do this for current mode control also, but again this validation will not come in the exam or the assignment, but one should know how to validate the model, but it is important to know, how to model in MATLAB those things will be there, but the validation itself will not be asked in the assignment or the exam case study, that is it for today.

Thank you very much.